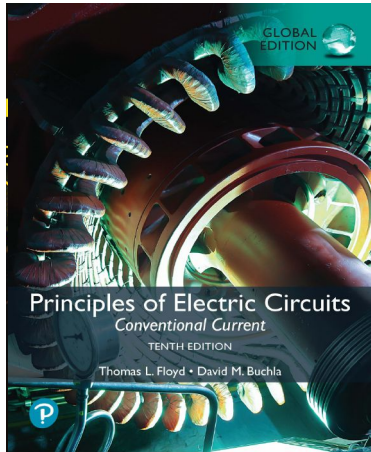


# Principles of Electric Circuits: Conventional Current

Tenth Edition, Global Edition



## Chapter 14


Inductors



Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved
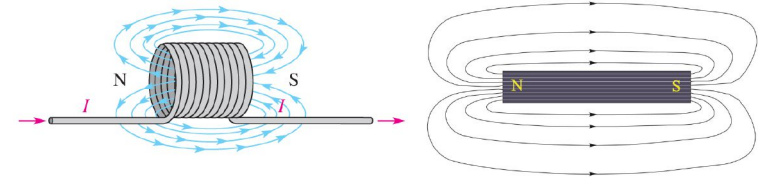
## Summary: Inductance (1 of 3)

Inductance is the property of a conductor to oppose a *change* in current. The effect of inductance is greatly magnified by winding a coil on a magnetic material. When there is current in the coil, a magnetic field is generated, similar to that of a bar magnet.



Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved

## Summary: Self Inductance (2 of 3)

Self-inductance is usually just called inductance, symbolized by  $L$ . Self-inductance is a measure of a coil's ability to establish an induced voltage as a result of a *change* in its current.

The unit of inductance is the **henry (H)**. One henry is the inductance of a coil when a current, changing at a rate of one ampere per second, induces one volt across the coil.

This induced voltage is given by the formula  $v_{\text{ind}} = L \frac{di}{dt}$

where

$v_{\text{ind}}$  = induced voltage in volts

$L$  = inductance in henries

$\frac{di}{dt}$  = rate of change of current in amperes per second



Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved

## Summary: Self Inductance (3 of 3)

Example:

What is the inductance if 10.3 mV is induced across a coil if the current is changing at a rate of 680 mA/s?

$$v_{\text{ind}} = L \frac{di}{dt}$$

$$L = \frac{v_{\text{ind}}}{\frac{di}{dt}} = \frac{10.3 \text{ mV}}{680 \text{ mA/s}} = 15.1 \text{ mH}$$

Question:

What will happen if the rate of change of current increases?

The induced voltage will increase, opposing the change in current.




Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved
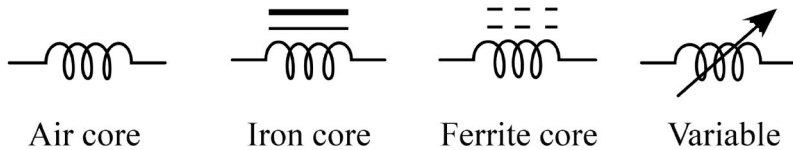
## Physical characteristics of inductors

An inductor is basically a coil of wire that surrounds a magnetic or nonmagnetic material called the **core**. Examples of magnetic materials are iron, nickel, steel, cobalt, or alloys. Inductor symbols are based on the core material.

Common symbols for inductors (coils) are:



## Summary: Factors affecting inductance (1 of 3)

The inductance of a coil is dependent upon four factors:  $L = \frac{N^2 \mu A}{l}$

where


$L$  = inductance in henries

$N$  = number of turns of wire

$\mu$  = permeability in H/m (same as Wb/At·m)

$A$  = cross-sectional area

$l$  = coil length on meters

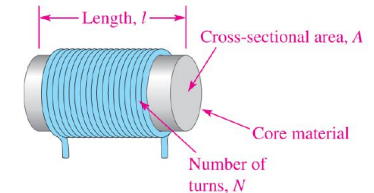

Permeability varies greatly with different materials; high permeability cores can increase the inductance by thousands of times over air.

## Summary: Factors affecting inductance (2 of 3)


### Example

What is the inductance of a 2.0 cm long, 150 turn coil wrapped on an low carbon steel core that is 0.50 cm diameter? The permeability of low carbon steel is  $2.5 \times 10^{-4}$  H/m (Wb/At·m).

$$\begin{aligned}
 L &= \frac{N^2 \mu A}{l} \\
 &= \frac{(150)^2 (2.5 \times 10^{-4} \text{ Wb/At}\cdot\text{m})(1.96 \times 10^{-5} \text{ m}^2)}{0.020 \text{ m}} \\
 &= 5.52 \text{ mH}
 \end{aligned}$$
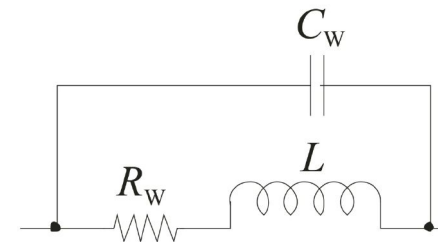
## Summary: Factors affecting inductance (3 of 3)

The inductance given by the equation in the previous slide is for the ideal case. In practice, inductors have winding resistance ( $R_w$ ) and winding capacitance ( $C_w$ ). An equivalent circuit for a practical inductor including these effects is:



## Summary: Faraday's law (review)

Recall that Faraday's law can be written as  $v_{\text{ind}} = N \left( \frac{d\phi}{dt} \right)$ .


Faraday's law states that the induced voltage across a coil is equal to the number of turns (loops) times the rate of flux *change*. The key term here is *change*.

Lenz's law added the concept that the polarity of the induced voltage is such that it *opposes* the change. Thus, if a current in a coil tries to change the flux, a voltage is generated to oppose that change.
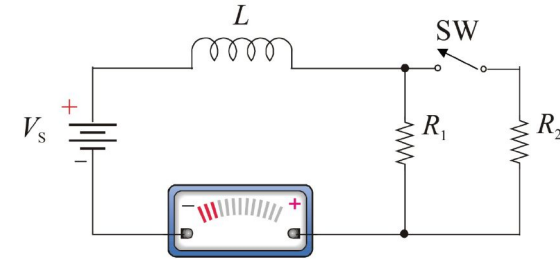
## Summary: Lenz's law (1 of 3)


The effect of a change in current is illustrated below:

Initially, the SW is open and there is a small current in the circuit through  $L$  and  $R_1$  as indicated on the meter.



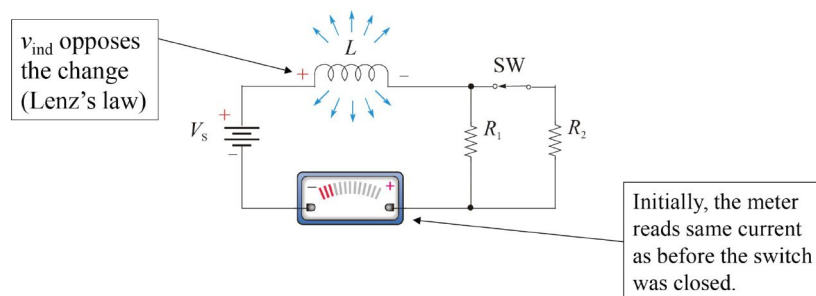
## Summary: Lenz's law (2 of 3)

SW closes and immediately a voltage appears across  $L$  that tends to oppose any *change* in current.



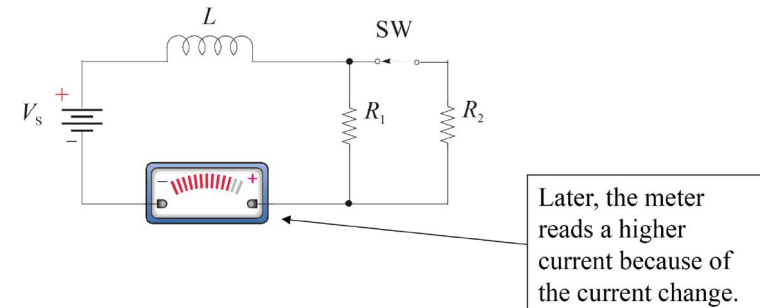
## Summary: Lenz's law (3 of 3)

After a time, the current stabilizes at a higher level (due to  $I_2$ ) as the voltage decays across the coil.


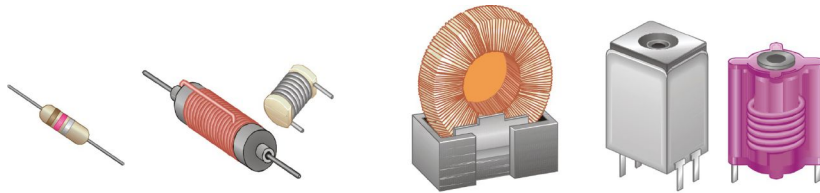
## Summary: Practical inductors

Inductors come in a variety of sizes. A few common ones are shown here.



Encapsulated   Wirewound (high current)   Torroid coil   Variable


## Summary: Series inductors

When inductors are connected in series, the total inductance is the sum of the individual inductors. The general equation for inductors in series is

$$L_T = L_1 + L_2 + L_3 + \dots L_n$$
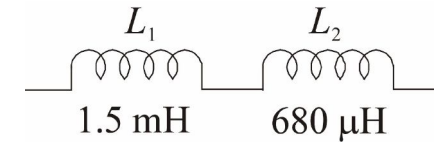
### Example

If a 1.5 mH inductor is connected in series with an 680 mH inductor, the total inductance is **2.18 mH**



## Summary: Parallel inductors (1 of 2)

When inductors are connected in parallel, the total inductance is smaller than the smallest one. The general equation for inductors in parallel is

$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}}$$

The total inductance of two inductors is


$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

...or you can use the product-over-sum rule with two inductors.

## Summary: Parallel inductors (2 of 2)



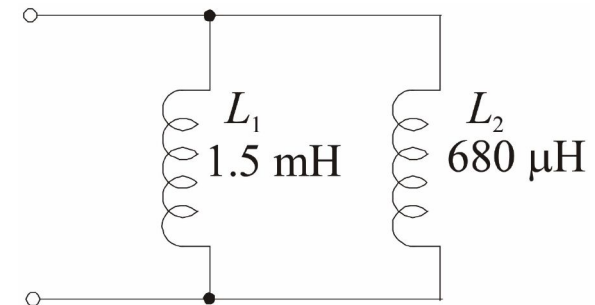
### Example

If a 1.5 mH inductor is connected in parallel with an 680 μH inductor, the total inductance is **468 μH**



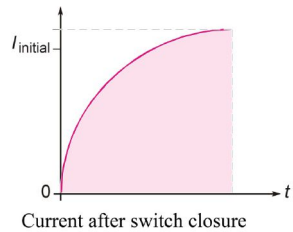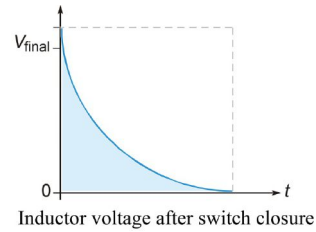
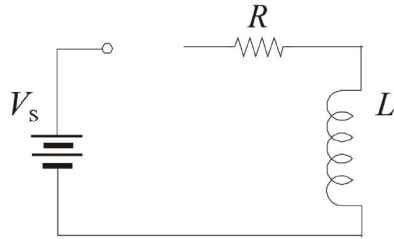
## Summary: Inductors in dc circuits (1 of 2)

When an inductor is connected in series with a resistor and dc source, the current change is exponential.


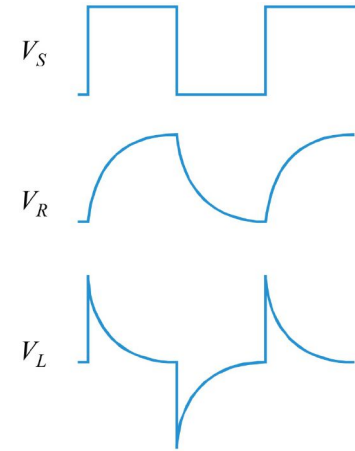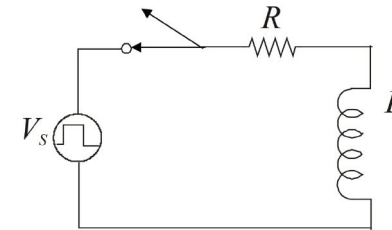
## Summary: Inductors in dc circuits (2 of 2)

The same shape curves are seen if a square wave is used for the source.




## Summary: Universal exponential curves (1 of 5)

Specific values for current and voltage can be read from a universal curve. For an  $RL$  circuit, the time constant is

$$\tau = \frac{L}{R}$$

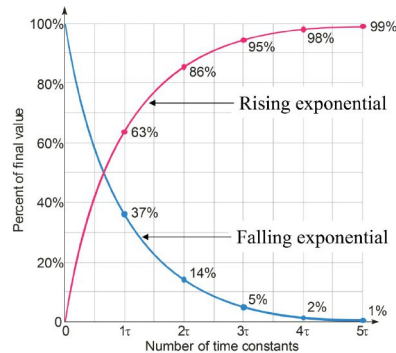For the rising exponential,  $5\tau$  is typically considered to be 100%. For the falling exponential,  $5\tau$  is typically considered to be 0%.




## Summary: Universal exponential curves (2 of 5)

The curves can give specific information about an  $RL$  circuit.
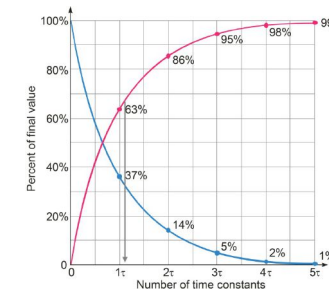
### Example

In a series  $RL$  circuit, when is  $V_R > 2V_L$ ?

Read the rising exponential at the 67% level. After  $1.1\tau$



## Summary: Universal exponential curves (3 of 5)

### Example

Plot the normalized universal exponential curves on the T I-84 Plus CE calculator.

The equations for a rising and falling exponential curves are

$$y = 1 - e^{-x} \quad (\text{rising})$$

$$y = -e^{-x} \quad (\text{falling})$$

Graph parameters are shown

```
ENG FLOAT AUTO a+bI RADIAN MP
WINDOW
Xmin=0
Xmax=5.28
Xscl=1
Ymin=0
Ymax=1
Yscl=0.1
Xres=1
ΔX=0.02
TraceStep=0.04
```

## Summary: Universal exponential curves (4 of 5)

### Example


Plot the normalized universal exponential curves on the T I-84 Plus CE calculator.

The equations for a rising and falling exponential curves are

$$y = 1 - e^{-x} \quad (\text{rising})$$

$$y = -e^{-x} \quad (\text{falling})$$

The graph is

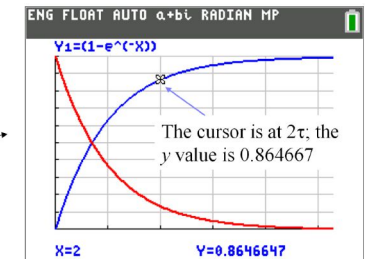

## Summary: Universal exponential curves (5 of 5)

The universal curves can be applied to general formulas for the current (or voltage) curves for  $RL$  circuits. The general current formula is

$$i = I_F + (I_i - I_F)e^{-Rt/L}$$

$I_F$  = final value of current

$I_i$  = initial value of current

$i$  = instantaneous value of current

The final current is greater than the initial current when the inductive field is building, or less than the initial current when the field is collapsing.

## Summary: Inductive reactance

Inductive reactance is the opposition to ac by an inductor. The equation for inductive reactance is


$$X_L = 2\pi fL$$

### Examples

- The reactance of a 33 mH inductor when a frequency of 550 kHz is applied is **114  $\Omega$**
- What size inductor will have a reactance of 10 kW at 40 MHz? **39.8  $\mu\text{H}$**
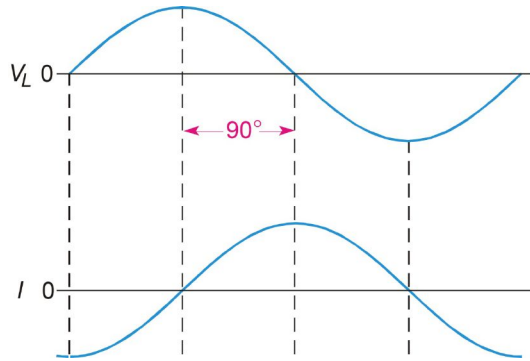
## Summary: Inductive phase shift

When a sine wave is applied to an inductor, there is a phase shift between voltage and current such that voltage always leads the current by  $90^\circ$ .



## Summary: Power in an inductor

**True Power:** Ideally, inductors do not dissipate power. However, a small amount of power is dissipated in the winding resistance, given by the equation:

$$P_{\text{true}} = (I_{\text{rms}})^2 R_w$$

**Reactive Power:** Reactive power is a measure of the rate at which the inductor stores and returns energy. One form of the reactive power equation is:

$$P_r = V_{\text{rms}} I_{\text{rms}}$$

The unit for reactive power is the VAR.

## Summary: Q of an inductor

The **quality factor (Q)** for an inductor is given by the ratio of reactive power to true power. Note that Q is defined only at a specific frequency because  $X_L$  is frequency dependent.

$$Q = \frac{I^2 X_L}{I^2 R_w}$$

For a series circuit,  $I$  cancels, leaving

$$Q = \frac{X_L}{R_w}$$

## Key Terms (1 of 2)

- Inductor** An electrical device, formed by a wire wound around a core, having the property of inductance; also known as a coil.
- Winding** The loops or turns of wire in an inductor.
- Induced voltage** Voltage produced as a result of a changing magnetic field.
- Inductance** The property of an inductor whereby a change in current causes the inductor to produce a voltage that opposes the change in current.

## Key Terms (2 of 2)

- Henry (H)** The unit of inductance.
- RL time constant** A fixed time interval, set by the  $L$  and  $R$  values, that determines the time response of a circuit. It equals the ratio of  $L/R$ .
- Inductive reactance** The opposition of an inductor to sinusoidal current. The unit is the ohm.
- Quality factor** The ratio of reactive power to true power for an inductor.

## Quiz (1 of 11)

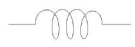
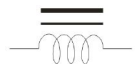

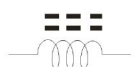
1. Assuming all other factors are the same, the inductance of an inductor will be larger if
- more turns are added
  - the area is made larger
  - the length is shorter
  - all of the above

## Quiz (2 of 11)

2. The henry is defined as the inductance of a coil when
- a constant current of one amp develops one volt.
  - one volt is induced due to a change in current of one amp per second.
  - one amp is induced due to a change in voltage of one volt.
  - the opposition to current is one ohm.

## Quiz (3 of 11)



3. The symbol for a ferrite core inductor is

- a. 
- b. 
- c. 
- d. 



### Quiz (4 of 11)

4. The symbol for a variable inductor is

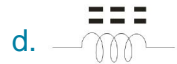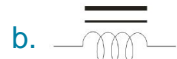

### Quiz (5 of 11)

5. The total inductance of a  $270\ \mu\text{H}$  inductor connected in series with a  $1.2\ \text{mH}$  inductor is

- a.  $220\ \mu\text{H}$
- b.  $271\ \mu\text{H}$
- c.  $599\ \mu\text{H}$
- d.  $1.47\ \mu\text{H}$

### Quiz (6 of 11)

6. The total inductance of a  $270\ \mu\text{H}$  inductor connected in parallel with a  $1.2\ \text{mH}$  inductor is

- a.  $220\ \mu\text{H}$
- b.  $271\ \mu\text{H}$
- c.  $599\ \mu\text{H}$
- d.  $1.47\ \mu\text{H}$

### Quiz (7 of 11)


7. When an inductor is connected through a series resistor and switch to a dc voltage source, the voltage across the resistor after the switch closes has the shape of

- a. a straight line
- b. a rising exponential
- c. a falling exponential
- d. none of the above

### Quiz (8 of 11)

8. For circuit shown, the time constant is

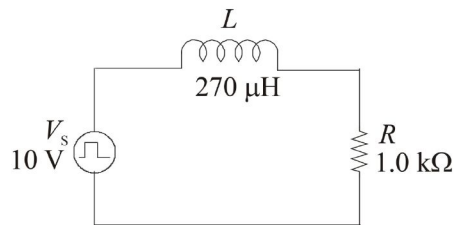
- a. 270 ns
- b. 270  $\mu$ s
- c. 270 ms
- d. 3.70 s



### Quiz (9 of 11)

9. For circuit shown, assume the period of the square wave is 10 times longer than the time constant. The shape of the voltage across L is

- a.
- b.
- c.
- d.

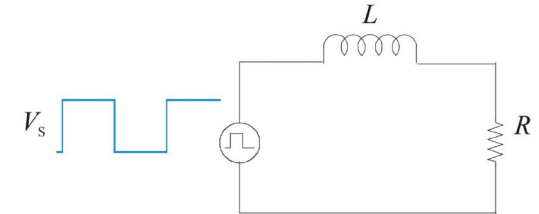

### Quiz (10 of 11)

10. If a sine wave from a function generator is applied to an inductor, the current will

- a. lag voltage by  $90^\circ$
- b. lag voltage by  $45^\circ$
- c. be in phase with the voltage
- d. none of the above

### Quiz (11 of 11)

Answers:

- 1. d
- 2. b
- 3. d
- 4. c
- 5. d
- 6. a
- 7. b
- 8. a
- 9. c
- 10. a