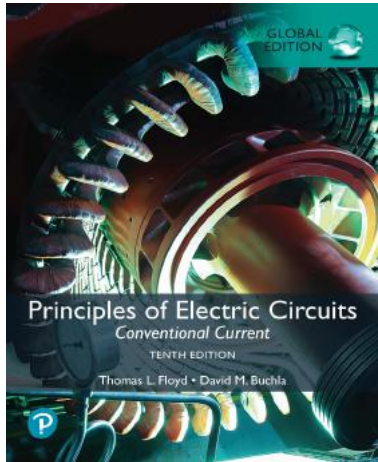


# Principles of Electric Circuits: Conventional Current

Tenth Edition, Global Edition




## Chapter 18 Passive Filters



Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved
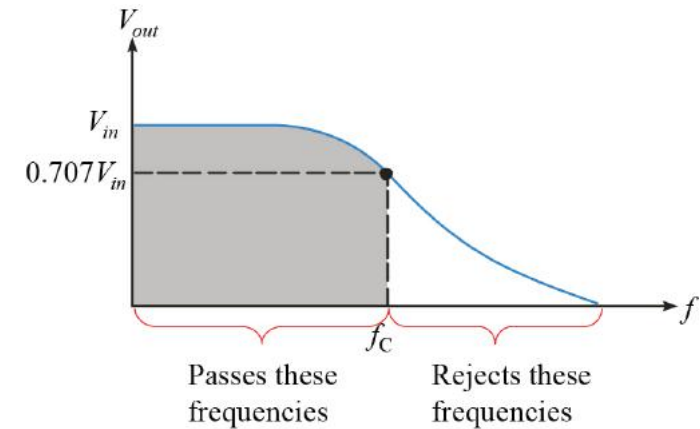
## Summary: Low-pass filters (1 of 2)

A low-pass filter allows signals with lower frequencies to pass while rejecting higher frequencies.




Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved
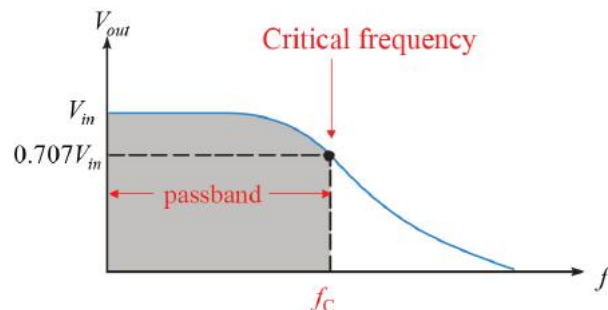
## Summary: Low-pass filters (2 of 2)

The **passband** is defined as range of frequencies passed by a filter within a specified limit.

The **critical frequency** (also called the cutoff frequency, or  $-3\text{dB}$  frequency) is the frequency at which the output voltage is 70.7% of the maximum.



Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved

## Summary: Decibels

Filter responses shown in plots and specifications are usually written in decibels, which is defined as

$$\text{dB} = 10 \log \left( \frac{P_{out}}{P_{in}} \right)$$

Another useful definition for the decibel, when measuring voltages across the same impedance, is

$$\text{dB} = 20 \log \left( \frac{V_{out}}{V_{in}} \right)$$

Because it is a ratio, the decibel is dimensionless.




Copyright © 2022, 2010, 2007 Pearson Education, Ltd. All Rights Reserved
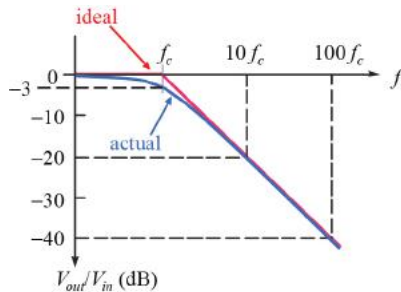
## Summary: Bode plot (1 of 2)


A Bode magnitude plot is a semilog response curve for a filter (log on x and decibels on y). For example, a basic low-pass filter ideally has the Bode plot shown. Actual filters roll-off to  $-3\text{dB}$  at  $f_c$ .

The roll-off rate of a basic  $RC$  or  $RL$  filter is  $-20\text{ dB per decade}$ .



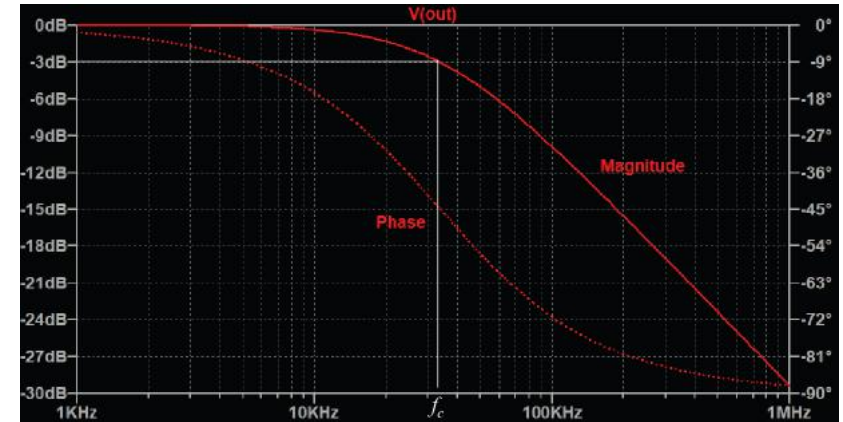
## Summary: Bode plot (2 of 2)

The second type of Bode plot is a phase plot. This LTSpice plot shows both the magnitude and phase plot for the text Example 18-6.



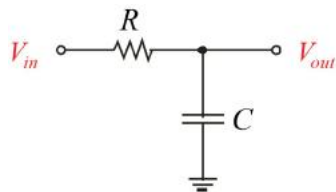
## Summary: Low-pass filter circuits (1 of 3)

A basic low-pass filter can be constructed from either  $RC$  or  $RL$  components. The critical frequency for either type is found by setting  $X = R$ .



$RC$  low-pass filter
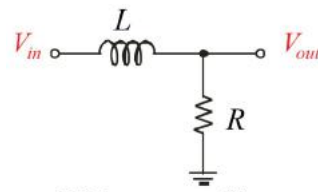
$$\text{For the } RC \text{ circuit, } f_c = \frac{1}{2\pi RC}$$




$RL$  low-pass filter

$$\text{For the } RL \text{ circuit, } f_c = \frac{1}{2\pi (L/R)}$$

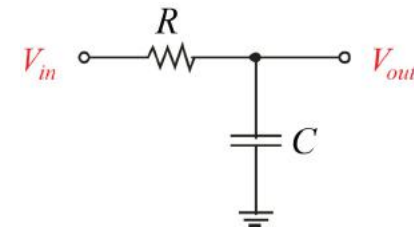
## Summary: Low-pass filter circuits (2 of 3)

The output voltage of a low-pass filter at any frequency can be derived from the voltage-divider equation.



For the  $RC$  circuit,
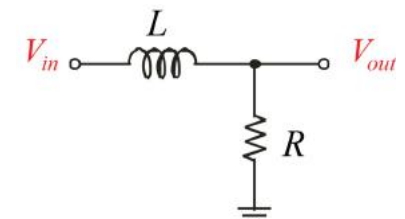
$$V_{out} = \left( \frac{X_C}{\sqrt{R^2 + X_C^2}} \right) V_{in}$$



For the  $RL$  circuit,


$$V_{out} = \left( \frac{R}{\sqrt{R^2 + X_L^2}} \right) V_{in}$$

## Summary: Low-pass filter circuits (3 of 3)

The basic  $RC$  and  $RL$  low-pass circuits are both lag networks. At the critical frequency the phase shift is  $-45^\circ$  for both circuits.



Phase response for both circuits:

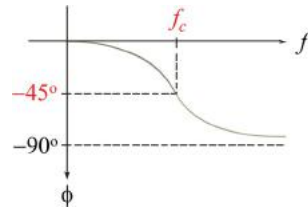


## Summary: LTSpice

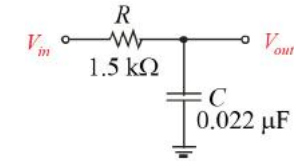
### Example

Determine  $f_c$  for the circuit.

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi (1.5\text{k}\Omega)(0.022\ \mu\text{F})} = 4.82\ \text{kHz}$$



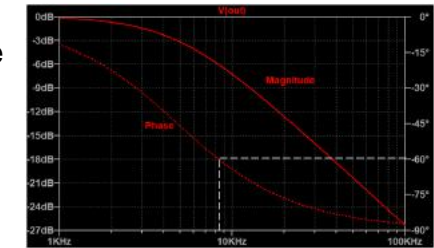You can view the Bode plot using either LTSpice or Multisim. Here is the LTSpice file for the circuit.




### Question:

At what frequency is the phase shift  $-60^\circ$ ? 8.4 kHz

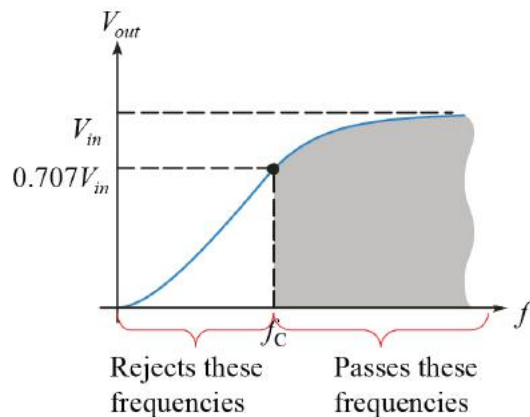
## Summary: High-pass filters (1 of 6)

A high-pass filter allows signals with higher frequencies to pass while rejecting lower frequencies.




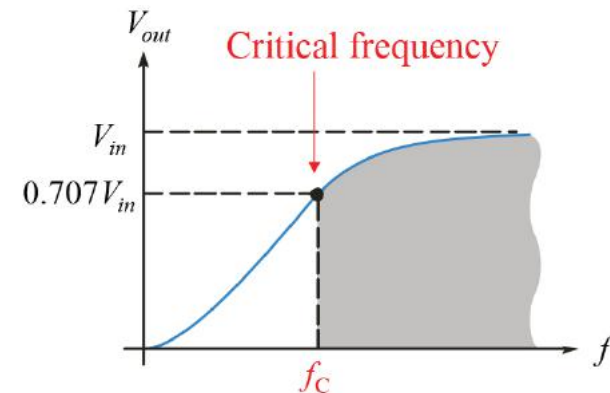
## Summary: High-pass filters (2 of 6)

The **critical frequency** is the same as in the low-pass case, namely the frequency at which the output voltage is 70.7% of the maximum.


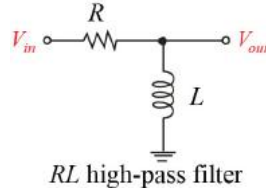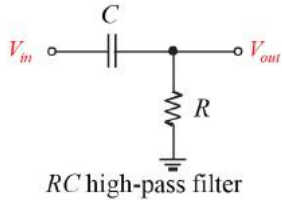
## Summary: High-pass filters (3 of 6)

As with low-pass filters, a basic high-pass filter can be constructed from either  $RC$  or  $RL$  components. The critical frequency for either type is found by setting  $X = R$  and is the same as the low-pass  $f_c$ .




For the  $RC$  circuit,  $f_c = \frac{1}{2\pi RC}$

For the  $RL$  circuit,  $f_c = \frac{1}{2\pi(L/R)}$

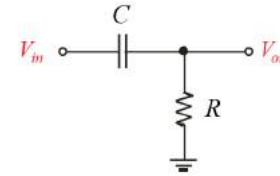
## Summary: High-pass filters (4 of 6)

The output voltage of a high-pass filter at any frequency can also be derived from the voltage-divider equation.



For the  $RC$  circuit,
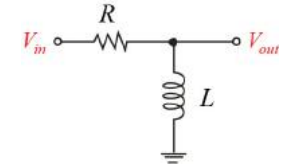
$$V_{out} = \left( \frac{R}{\sqrt{R^2 + X_C^2}} \right) V_{in}$$





For the  $RL$  circuit,


$$V_{out} = \left( \frac{X_L}{\sqrt{R^2 + X_L^2}} \right) V_{in}$$
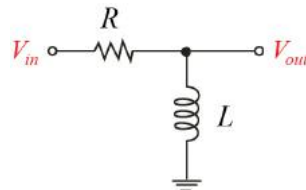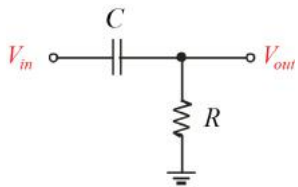
## Summary: High-pass filters (5 of 6)

The basic  $RC$  and  $RL$  high-pass circuits are both lead networks. At the critical frequency, the phase shift is  $+45^\circ$  for both circuits.



Phase response for both circuits:

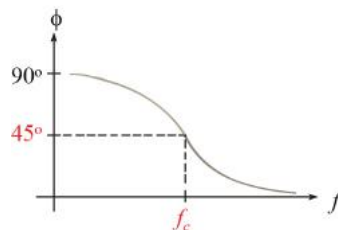


## Summary: High-pass filters (6 of 6)

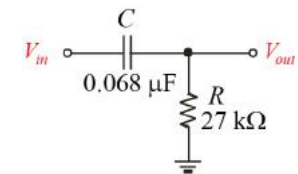
### Example

Determine  $f_c$  for the circuit.

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi (27 \text{ k}\Omega)(0.068 \text{ }\mu\text{F})} = 86.7 \text{ Hz}$$




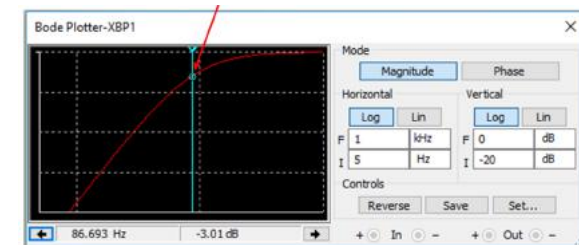You can view the Bode plot using either LTSpice or Multisim. Here is the Multisim result. The cursor is at  $f_c$ , confirming the calculation.



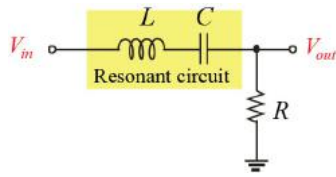
## Summary: Band-pass filter circuits (1 of 2)

Basic band-pass filter circuits can be constructed from a combination of low-pass and high-pass filters or using resonant circuits.




Series resonant band-pass filter

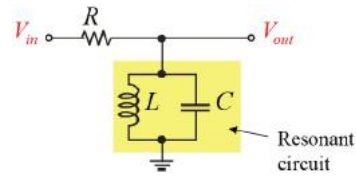

Parallel resonant band-pass filter
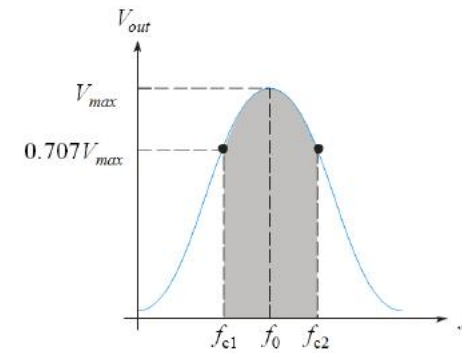
## Summary: Band-pass filter circuits (2 of 2)


A generalized response for a band-pass filter is shown.




The bandwidth is measured between the frequencies where the output drops to  $0.707V_{max}$ .
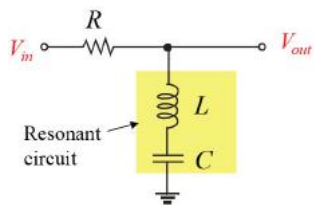
## Summary: Band-stop filter circuits (1 of 4)

Basic band-stop filter circuits can also be constructed from a combination of low-pass and high-pass filters or using resonant circuits. Resonant band-stop filters are shown.



Series resonant band-stop filter

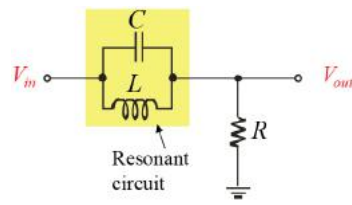


Parallel resonant band-stop filter
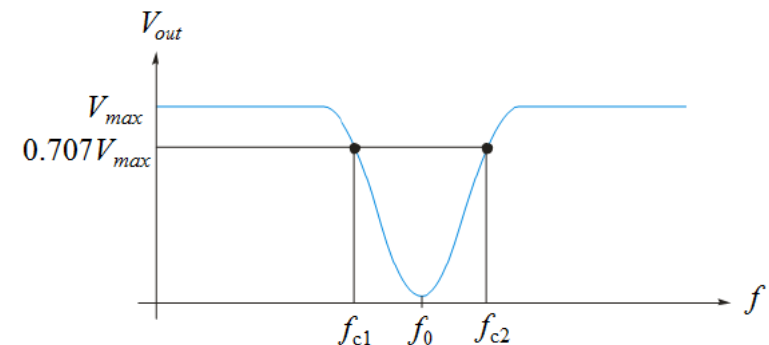
## Summary: Band-stop filter circuits (2 of 4)

A generalized response for a band-stop filter is shown.


The bandwidth is measured between the frequencies where the output drops to  $0.707V_{max}$ .


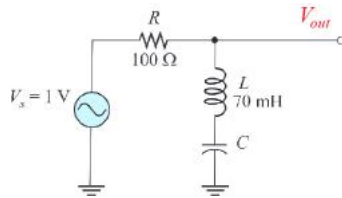
## Summary: Band-stop filter circuits (3 of 4)

A series resonant notch filter is shown.  $R_W$  for the inductor is  $10\ \Omega$ . What value of  $C$  is required to reject  $60\ \text{Hz}$ ?


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
$$C = \left(\frac{1}{2\pi\sqrt{L}f_0}\right)^2 = \left(\frac{1}{2\pi\sqrt{70\ \text{mH}}(60\ \text{Hz})}\right)^2 = 101$$



The following slide shows the Bode plot from an LTSpice calculation.

## Summary: Band-stop filter circuits (4 of 4)

LTSpice simulation:

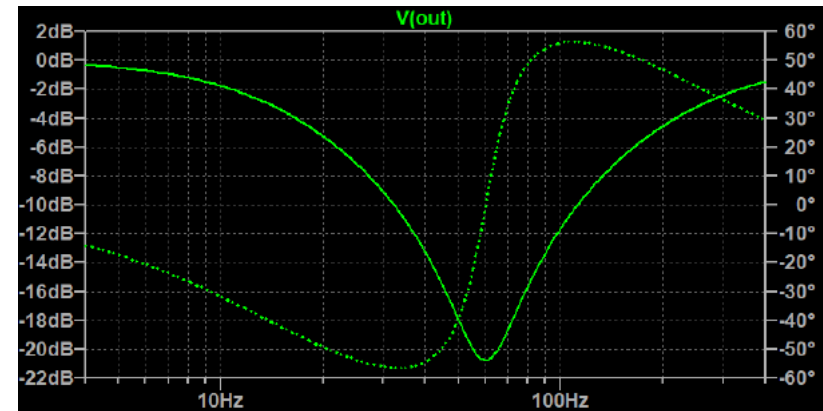

## Summary: Key ideas (1 of 2)

- Basic low-pass and high-pass filters are formed from  $RC$  or  $RL$  circuits.
- With low-pass filters, the output lags the input.
- With high-pass filters, the output leads the input.
- The roll off rate of basic low-pass or high-pass filters is  $-20\text{dB/decade}$ .
- A band-pass filter passes frequencies between two critical frequencies and rejects all others.

## Summary: Key ideas (2 of 2)

- A band-stop filter rejects frequencies between two critical frequencies and passes all others.
- Band-pass and band-stop filters can be made from both series and parallel resonant circuits.
- The bandwidth of a resonant filter is determined by the  $Q$  and the resonant frequency.
- The output voltage at a critical frequency is 70.7% of the maximum.

## Key ideas (1 of 3)

**Low-pass filter** A type of filter that passes all frequencies below a critical frequency and rejects all frequencies above that critical frequency.

**Passband** The range of frequencies passed by a filter.

**Critical frequency ( $f_c$ )** The frequency at which a filter's output voltage is 70.7% of the maximum.

**Roll-off** The rate of decrease of a filter's frequency response.

## Key ideas (2 of 3)

**Attenuation** A reduction of the output signal compared to the input signal, resulting in a ratio with a value less than 1 for the output voltage to the input voltage for a circuit.

**Decade** A tenfold change in the frequency or other parameter.

**Bode plot** A graph of a filter's frequency response showing the change in the output voltage to the input voltage ratio expressed in dB as a function of frequency for a constant input voltage.

## Key ideas (3 of 3)

**High-pass filter** A type of filter that passes all frequencies above a critical frequency and rejects all frequencies below that critical frequency.


**Band-pass filter** A filter that passes a range of frequencies lying between two critical frequencies and rejects the frequencies lying above and below that range.

**Center frequency** The resonant frequency of a band-pass or band-stop filter.

**Band-stop filter** A filter that rejects a range of frequencies lying between two critical frequencies and passes frequencies above and below that range.

## Quiz (1 of 11)

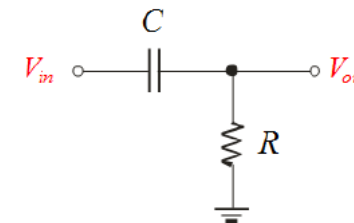
1. The basic filter circuit shown is a
  - a. low-pass
  - b. high-pass
  - c. band-pass
  - d. band-stop






## Quiz (2 of 11)

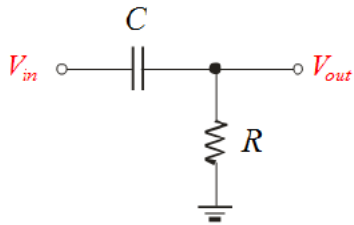2. For the circuit shown, the output voltage will
- lead the input voltage
  - lag the input voltage
  - be in phase with the input voltage
  - be out of phase with the input voltage



## Quiz (3 of 11)

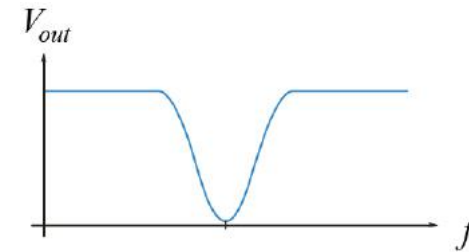3. A filter with the response shown is a
- low-pass filter
  - high-pass filter
  - band-pass filter
  - band-stop filter




## Quiz (4 of 11)

4. A series resonant filter can be made into a
- low-pass filter
  - high-pass filter
  - band-pass filter
  - none of the above

## Quiz (5 of 11)

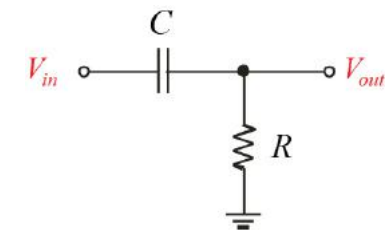5. For the circuit shown, the output voltage at any frequency can be expressed as

- $V_{out} = \left( \frac{R}{\sqrt{R^2 + X_C^2}} \right) V_{in}$
- $V_{out} = 0.707V_{max}$
- $V_{out} = \left( \frac{X_C}{\sqrt{R^2 + X_C^2}} \right) V_{in}$
- $V_{out} = 0.707V_{in}$






## Quiz (6 of 11)

6. At the critical frequency, the phase shift of a low-pass filter is
- a.  $0^\circ$
  - b.  $-45^\circ$
  - c.  $+45^\circ$
  - d. none of the above

## Quiz (7 of 11)

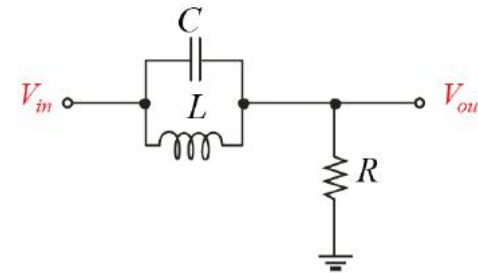7. The basic filter circuit shown is a
- a. low-pass
  - b. high-pass
  - c. band-pass
  - d. band-stop



## Quiz (8 of 11)

8. At the cutoff frequency, the output of a filter is
- a. equal to the input
  - b.  $-3$  dB
  - c.  $-6$  dB
  - d.  $-20$  dB

## Quiz (9 of 11)

9. The definition of a decibel is
- a.  $\text{dB} = 10 \log \left( \frac{P_{out}}{P_{in}} \right)$
  - b.  $\text{dB} = 20 \log \left( \frac{V_{out}}{V_{in}} \right)$
  - c. both a and b are correct
  - d. none of the above

## Quiz (10 of 11)

10. The measurement unit used with decibels is the

- a. watt
- b. volt
- c. ohm
- d. none of the above

## Quiz (11 of 11)

Answers:

- 1. b
- 2. a
- 3. d
- 4. c
- 5. a
- 6. b
- 7. d
- 8. b
- 9. c
- 10. d