



**T.C**

**ADANA ALPARSLAN TÜRKES  
SCIENCE AND TECHNOLOGY  
UNIVERSITY**

**FACULTY OF ENGINEERING**

**EEE 222 ELECTRICAL CIRCUIT  
LABORATORY II**

**2020-2021 Spring Term**

**Dr. Özgür ÇELİK**


**EXPERIMENT VI**

**FREQUENCY RESPONSE &  
RESONANT CIRCUITS**

## INTRODUCTION

In sinusoidal circuit analysis, voltages and currents are founded in a circuit with a constant frequency source. If the amplitude of the sinusoidal source remain constant and vary the frequency, the circuit's frequency response will be obtained. The frequency response of a circuit is the variation of the gain and phase in its behavior with change in signal frequency.


The transfer function  $\mathbf{H}(\omega)$  (network function) is used for finding the frequency response of a circuit with  $\omega$  varying from  $\omega=0$  to  $\omega=\infty$  and is a complex quantity with a magnitude  $H(\omega)$  and a phase  $\phi$ , defined in Figure 1.

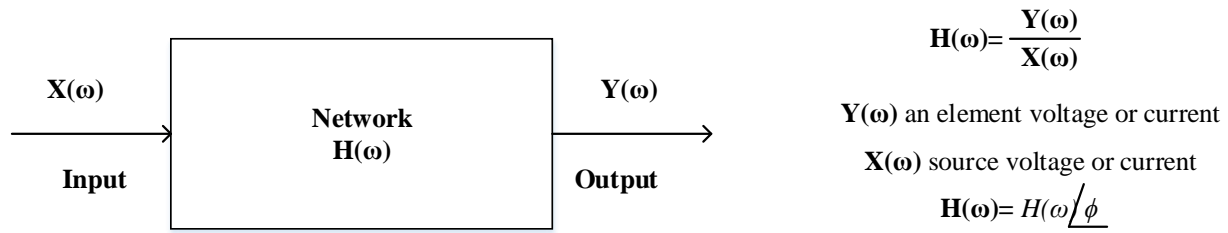

*Figure 1.* The transfer function.

The frequency response of an RLC circuit may cause resonance frequency occurs when the capacitive and inductive reactance cancel each other.

## PRELIMINARY WORK

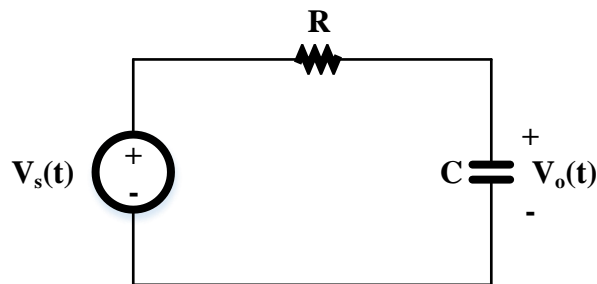


*Figure 2.* The RC circuit.

**P1** For the RC circuit given in Figure 2

- a) Obtain the transfer function  $V_o/V_s$  for  $V_s = V_m \cos \omega t$ .
- b) Draw the amplitude response and the phase response.
- c) According to the value of  $\omega/\omega_0$  as 0, 1, 2, 3, 10, 20, 100 and  $\infty$ , calculate the  $H$  and  $\phi$ .


d) Use LTSPICE to plot frequency response for  $V_m=10$  V,  $R=10$   $\Omega$  and  $L=4.7$  mH.

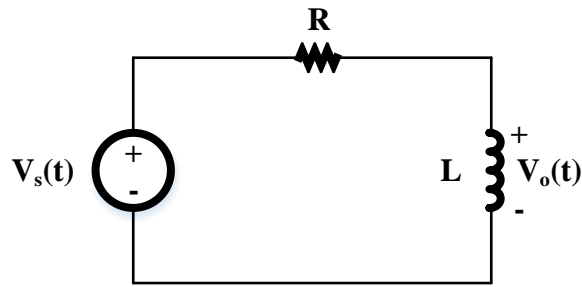

*Figure 3.* The RL circuit.

**P2** Repeat P1 from “a” to “c” for the circuit shown in Figure 3


a) Use LTSPICE to plot frequency response for  $V_m=10$  V,  $R=4.7$   $\Omega$  and  $L=4.7$  mH.

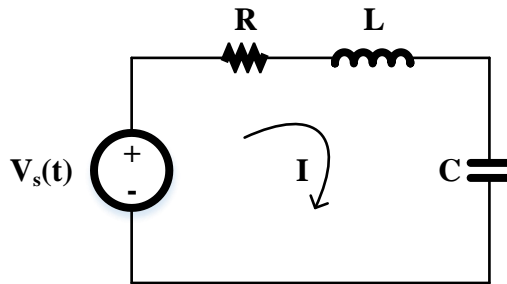

*Figure 4.* The series RLC circuit.

**P3** For the series RLC circuit given in Figure 4 for  $V_s=10\sin\omega t$   $R=2.2$   $\Omega$ ,  $L=100$   $\mu$ H and  $C=1000$   $\mu$ F

- Obtain the resonant frequency and the half-power frequencies.
- Calculate the quality factor and bandwidth.
- Determine the amplitude of the current at  $\omega_0$ ,  $\omega_1$  and  $\omega_2$ .
- Plot the current amplitude versus frequency
- Use LTSPICE to plot frequency response.

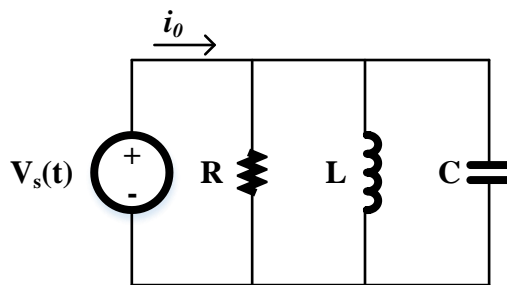

*Figure 5.* The parallel RLC circuit.

**P4** For the parallel RLC circuit given in Figure 5 for  $V_s=10\sin\omega t$   $R=2.2\ \Omega$ ,  $L=100\ \mu\text{H}$  and  $C=1000\ \mu\text{F}$

- Obtain the resonant frequency  $\omega_0$ , the quality factor  $Q$  and the bandwidth  $B$ .
- Calculate the half-power frequencies  $\omega_1$  and  $\omega_2$ .
- Determine the power consumption at  $\omega_0$ ,  $\omega_1$ , and  $\omega_2$ .
- Plot the current amplitude versus frequency
- Use LTSPICE to plot frequency response.

## EXPERIMENTAL WORK

- E1:** Build the circuit in figure 1 but make sure to measure the values of R and C beforehand.
- E1** Build the RC circuit in Figure 2 and fill the Table 1.

**Table 1.** The Output voltage and the phase angle for the RC circuit.

f (Hz)	V <sub>o</sub> (V)	V <sub>o</sub> /V <sub>s</sub>	ϕ (°)	f (Hz)	V <sub>o</sub> (V)	V <sub>o</sub> /V <sub>s</sub>	ϕ (°)
60				160			
70				170			
80				180			
90				190			
100				200			
110				210			
120				220			
130				230			
140				240			
150				250			

- E2** Build the RL circuit in Figure 3 and fill the Table 2.

**Table 2.** The Output voltage and the phase angle for the RL circuit.

f (Hz)	V <sub>o</sub> (V)	V <sub>o</sub> /V <sub>s</sub>	ϕ (°)	f (Hz)	V <sub>o</sub> (V)	V <sub>o</sub> /V <sub>s</sub>	ϕ (°)
60				160			
70				170			
80				180			
90				190			
100				200			
110				210			
120				220			
130				230			
140				240			
150				250			

**E3** Build the RLC circuit in Figure 4 and fill the Table 3.

**Table 3.** The current and the phase angle for the series RLC circuit.

<b>f (Hz)</b>	<b>I (A)</b>	<b>V<sub>m</sub>/R</b>	<b>φ (°)</b>	<b>f (Hz)</b>	<b>I (A)</b>	<b>V<sub>m</sub>/R</b>	<b>φ (°)</b>
6000				16000			
7000				17000			
8000				18000			
9000				19000			
10000				20000			
11000				21000			
12000				22000			
13000				23000			
14000				24000			
15000				25000			

**E4** Build the RLC circuit in Figure 5 and fill the Table 4.

**Table 4.** The current and the phase angle for the parallel RLC circuit.

<b>f (Hz)</b>	<b>I (A)</b>	<b>V<sub>m</sub>/R</b>	<b>φ (°)</b>	<b>f (Hz)</b>	<b>I (A)</b>	<b>V<sub>m</sub>/R</b>	<b>φ (°)</b>
6000				16000			
7000				17000			
8000				18000			
9000				19000			
10000				20000			
11000				21000			
12000				22000			
13000				23000			
14000				24000			
15000				25000			

**CONCLUSION**